

Code No:9AC48

Date: 09-August-2024 (FN)

B.Tech I-Year II- Semester External Examination, August-2024 (Regular & Supplementary)
BASIC ELECTRICAL AND ELECTRONICS ENGINEERING (CSE,IT,CS,AIIML,DS,IOT)

Time: 3 Hours

Max.Marks:60

Note: a) No additional answer sheets will be provided.
b) All sub-parts of a question must be answered at one place only, otherwise it will not be valued.
c) Missing data can be assumed suitably.

Bloom's Cognitive Levels of Learning (BCLL)

| | | | | | |
|------------|----|---------|----|----------|----|
| Remember | L1 | Apply | L3 | Evaluate | L5 |
| Understand | L2 | Analyze | L4 | Create | L6 |


Part - A

Max.Marks: 6x2=12

ANSWER ALL QUESTIONS, EACH QUESTION CARRIES 2 MARKS.

- 1 What is the current in 5 ohm Resistor?

BCLL L1 CO(s) CO1 Marks [2M]

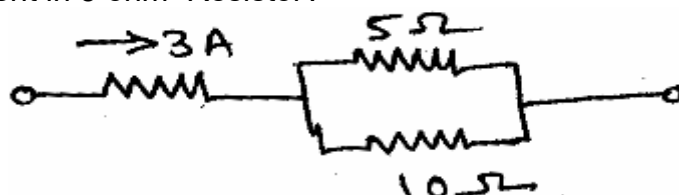

- 2 Write is the relationship between line phase values Voltage and current in delta connected three-phase, balanced system.
- 3 List the main parts of three phase induction motor?
- 4 Draw the V-I characteristics of PN Junction Diode .
- 5 List out the uses of BJT.
- 6 Write 2's complement of $(1000)_2$

L1 CO2 [2M]
L1 CO3 [2M]
L2 CO4 [2M]
L2 CO5 [2M]
L1 CO6 [2M]

Part – B

Max.Marks: 6x8=48

ANSWER ALL QUESTIONS. EACH QUESTION CARRIES 8 MARKS.

7. State Superposition Theorem and By using Superposition Theorem determine value of current (I) through 6 ohms resistor in the given circuit shown in Figure-1.

BCLL L3 CO(s) CO1 Marks [8M]

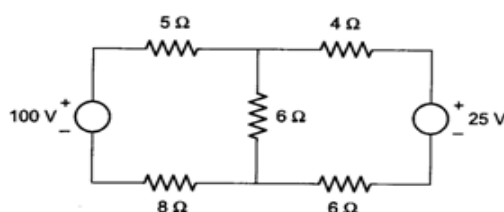


Figure-1.

OR

- 8 Explain basic construction and principle of operation of DC generator in detail with its applications.
9. i) Define the terms : a) cycle , b) Time period c) form factor d) Peak factor
ii) An alternating current is given by $i = 20 \sin 600t$ Amp. Calculate the frequency, peak value of current and the time taken t for the current to reach value of 10A.
- OR
- 10 An impedance $Z_1 = (2.4 + j3.2)$ ohm is in parallel with another impedance $Z_2 = (3-j4)$ ohm .The combination is given a supply of 200V. Calculate the total impedance, current supplied by source, current through individual branches, power factor and power consumed in the circuit.

L2 CO1 [8M]
L2 CO2 [8M]
L3
L3 CO2 [8M]

- | | | | | |
|----|---|----------|-----|------|
| 11 | i) Explain the concept of Faraday's laws. ii) Explain the principle of operation of three phase induction motor. | L2 L2 | CO3 | [8M] |
| OR | | | | |
| 12 | i) List out the classification of measuring instruments. ii) Compare Moving coil Instruments and moving Iron Instruments in any four aspects. | L2 L2 | CO3 | [8M] |
| 13 | i) Describe the operation of full wave rectifier with neat sketch and its wave forms. (ii) Explain the operation of PN junction diode in forward bias and reverse bias mode. | L2 L2 | CO4 | [8M] |
| OR | | | | |
| 14 | i) Describe the VI-characteristics of Zener diode under reverse biased mode. ii) Write short notes on clippers and clamps. | L2 L2 | CO4 | [8M] |
| 15 | Explain the input and output characteristics of the transistor in Common base configuration with diagrams. | L3 | CO5 | [8M] |
| OR | | | | |
| 16 | Explain the construction and working operation of n channel JFET. | L2 | CO5 | [8M] |
| 17 | i) Convert the following numbers : (a) $(FE7)_{16} = ()_{10}$ (b) $(753)_{10} = ()_8$ ii) Describe about weighted and unweighted codes. | L3 L2 | CO6 | [8M] |
| OR | | | | |
| 18 | Draw the different logic gates with truth tables. | L2 | CO6 | [8M] |

-- 00 -- 00 --